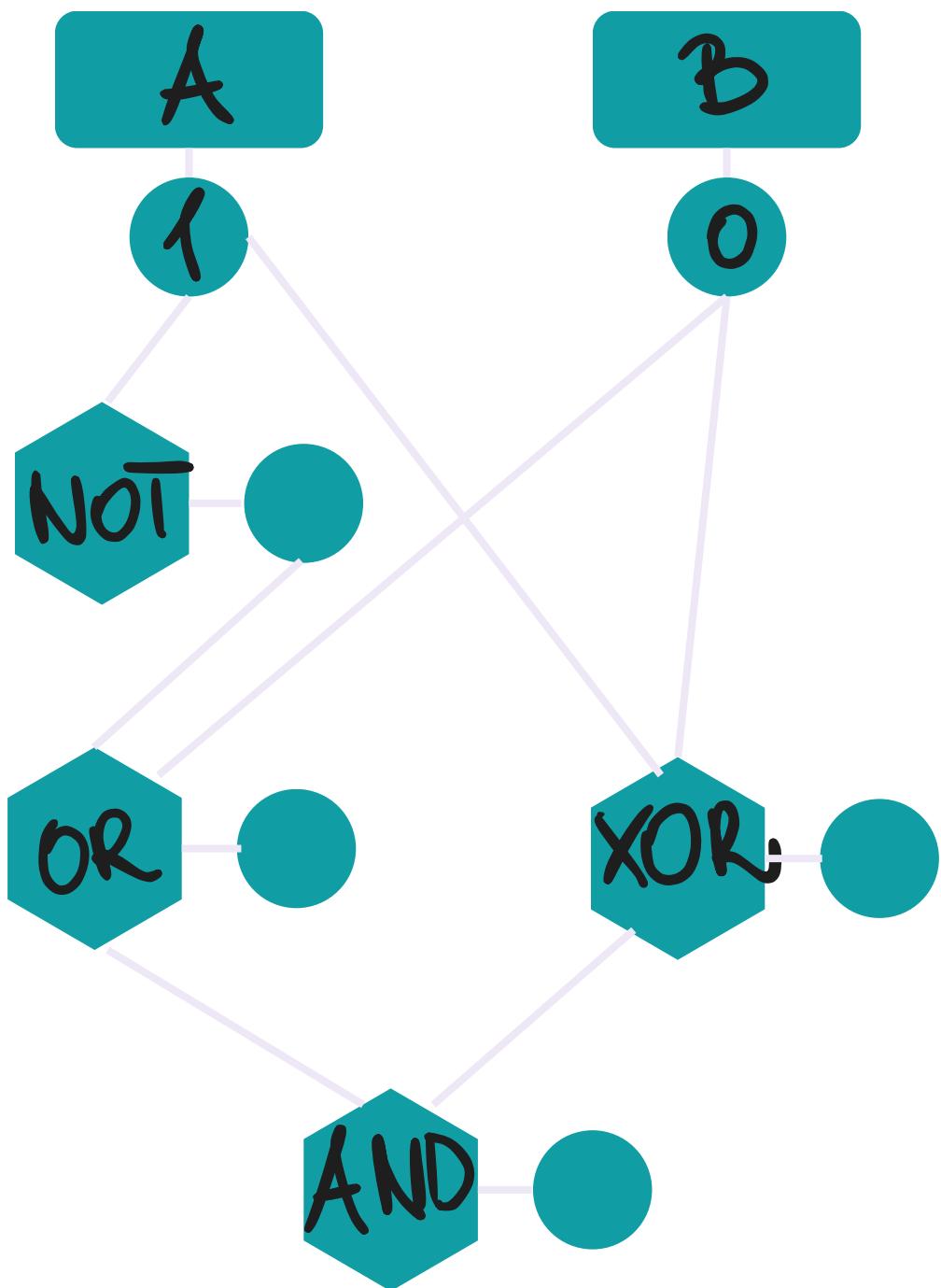


CRACK THE CODE #2



Instructions: Your goal is to discover the final output. Follow the path of signals A and B through the logic gates. Keep these rules in mind:

NOT: Inverts the signal (turns 1 into 0, and 0 into 1).


OR: Output is 1 if at least one input is 1.

XOR: Output is 1 only if the inputs are different (e.g., 1 and 0).

AND: Output is 1 only if both inputs are 1.

Quick Tip: Write the intermediate results in the small circles next to each gate so you don't get lost!

THE SOLUTION

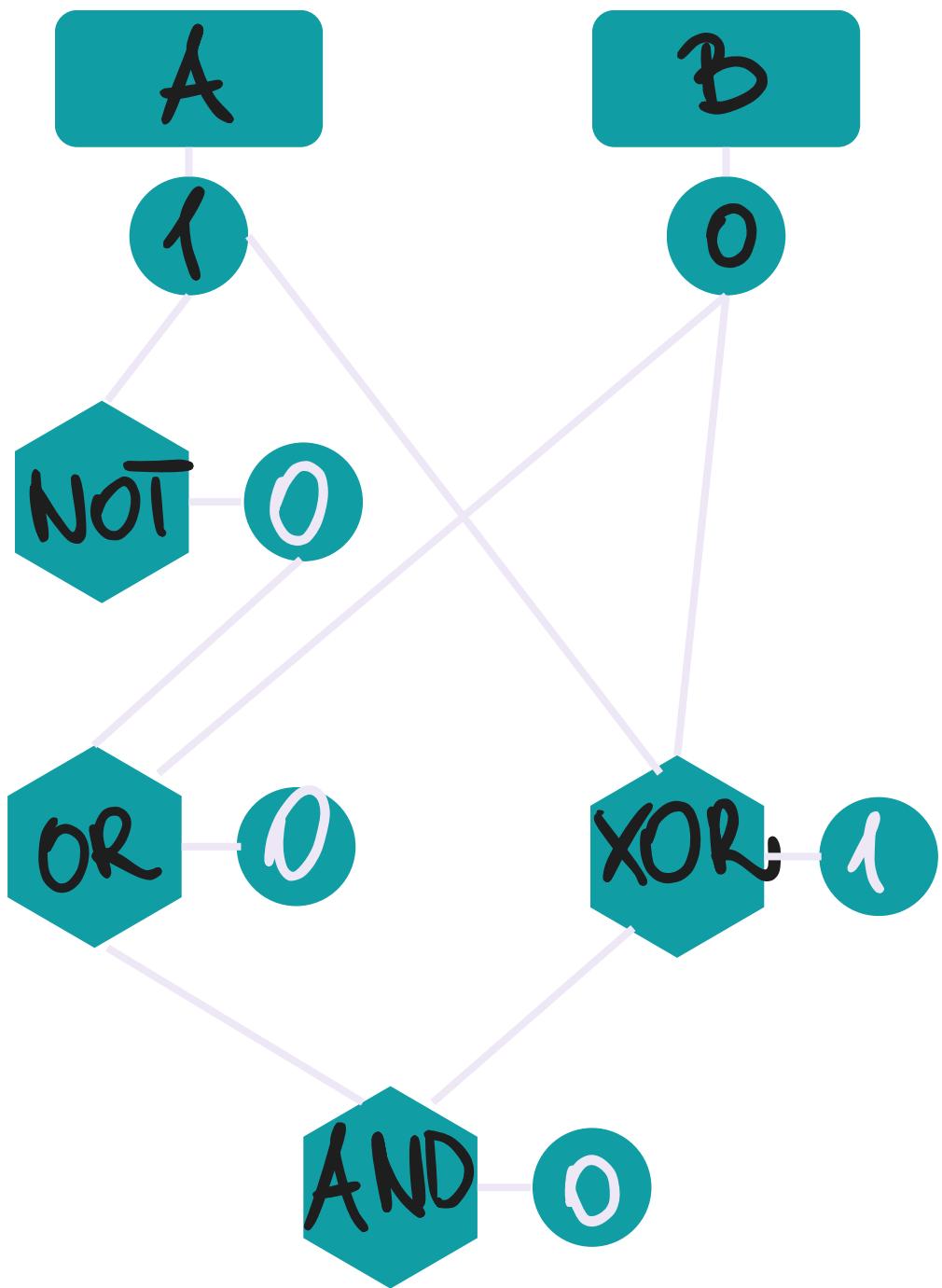

Logic Path:

NOT: Input signal A (1) changes to 0.

OR: Receives 0 (from the NOT gate) and 0 (directly from signal B). Result = 0.

XOR: Receives the original signals A (1) and B (0). Since they are different, the result = 1.

AND (Final): Receives the results from the previous gates: 0 and 1. For an AND gate, this is not enough to produce a 1.

FINAL OUTPUT: 0